

Lab Experiments for DC Circuits

Wayne M. Hope

**Formulations Media Inc
Edmonton / Alberta / Canada**

Table of Contents

1	DC Resistance Measurements
2	DC Voltage Measurements
3	DC Current Measurements
4	Ohm's Law
5	Series DC Circuits
6	Parallel DC Circuits
7	Series-Parallel DC Circuits
8	Voltage Divider Circuits
9	Thévenin's Theorem
10	Norton's Theorem
11	Superposition Theorem
12	Mesh Analysis
13	Maximum Power Transfer Theorem
14	The Wheatstone Bridge
15	DC Characteristics of Capacitors
16	DC Characteristics of Inductors