

# Lab Experiments for AC Circuits

**Wayne M. Hope**

Formulations Media Inc  
Edmonton / Alberta / Canada

## Table of Contents

1	Oscilloscope Voltage Measurements
2	Oscilloscope Time & Frequency Measurements
3	Oscilloscope Phase Measurements
4	AC Characteristics of Capacitors & Inductors
5	AC Series RC Circuits
6	AC Series RLC Circuits
7	AC Parallel RL Circuits
8	AC Parallel RLC Circuits
9	RC & RL Frequency Response
10	Transformer Characteristics
11	Series Resonant Circuits
12	Bandwidth & Q Measurements
13	Parallel Resonant Circuits
14	Bode Plots
15	Low Pass & High Pass Filters
16	Band Pass & Band Reject Filters