

# Lab Experiments for Devices

**Wayne M. Hope**

**Formulations Media Inc  
Edmonton / Alberta / Canada**

## Table of Contents

1	Diode Biasing
2	Other Diodes
3	Diode Rectifiers
4	Power Supply Filters
5	Diode Regulators
6	DC Transistor Characteristics
7	BJT Switching
8	Amplifier Basics
9	Common-Emitter Amplifiers
10	Emitter-Follower Amplifiers
11	Amplifier Frequency Response
12	Multistage Amplifiers
13	Power Amplifiers
14	FET Biasing
15	FET Amplifiers
16	DC Differential Amplifiers