

# Lab Experiments for Op Amps

**Wayne M. Hope**

**Formulations Media Inc  
Edmonton / Alberta / Canada**

## Table of Contents

1	Basic Op Amp Circuits
2	Op Amp Characteristics
3	Comparators & Multivibrators
4	Triggering Circuits
5	Op Amp Integrators
6	The 555 Timer
7	Active Filters
8	Op Amp Oscillators
9	Inverting Summer
10	Butterworth Filters
11	Difference Amplifiers
12	Bessel, Butterworth & Chebyshev Filters
13	Offset Compensation
14	Gain-Bandwidth Product
15	Sample-and-Hold Circuit
16	Single Supply Op Amps