

Problems in Devices

Wayne M. Hope

**Formulations Media Inc
Edmonton / Alberta / Canada**

Table of Contents

| | |
|----|--------------------------------|
| 1 | Semiconductors & Diodes |
| 2 | Diode Biasing |
| 3 | Rectifier & Filter Circuits |
| 4 | Bipolar Junction Transistors |
| 5 | BJT Biasing |
| 6 | Field-Effect Transistors |
| 7 | FET Biasing |
| 8 | Diode & Transistor Switching |
| 9 | Amplifier Measurement Concepts |
| 10 | h-Parameter Modeling |
| 11 | BJT Amplifier Analysis |
| 12 | FET Amplifier Analysis |
| 13 | Multi-Stage Amplifiers |
| 14 | Special Circuits |
| 15 | Negative Feedback Circuits |
| 16 | Multi-Layer Devices |

Answers to even questions are at
the end of each problem section