

Problems in Op Amps

Wayne M. Hope

**Formulations Media Inc
Edmonton / Alberta / Canada**

Table of Contents

- 1 Operational Amplifiers
- 2 Linear Op Amp Applications - Basic Circuits
- 3 Linear Op Amp Applications - Filter Circuits
- 4 Linear Op Amp Applications - Other Circuits
- 5 Non-Linear Op Amp Applications
- 6 Positive Feedback Circuits
- 7 Power Amplifiers
- 8 Power Supply Regulation
- 9 Analog to Digital (A/D) Conversion

Answers to even questions are at
the end of each problem section