

Table of Contents

1. VOLTAGE, CURRENT & RESISTANCE

1.1	Standards and Units	1-1
1.2	Number Systems.....	1-5
1.3	Prefixes.....	1-6
1.4	Unit Conversions.....	1-9
1.5	Voltage	1-12
1.6	Current.....	1-14
1.7	Resistance.....	1-16
1.8	Wire Tables	1-24
1.9	Temperature Effects	1-28
1.10	Measuring Voltage, Current and Resistance.....	1-30
1.11	Circuit Simulation.....	1-34
1.12	A Glance Back.....	1-35

2. OHM'S LAW, GRAPHS & POWER

2.1	Electric Circuits	2-2
2.2	Ohm's Law	2-4
2.3	Graphical Representations.....	2-9
2.4	Open Circuits.....	2-15
2.5	Power Calculations	2-18
2.6	System Efficiency.....	2-23
2.7	Troubleshooting.....	2-24
2.8	A Glance Back.....	2-27

3. SERIES DC CIRCUITS

3.1	Resistors in Series.....	3-2
3.2	Series Circuits.....	3-4
3.3	Kirchhoff's Voltage Law (KVL).....	3-7
3.4	Unloaded Voltage Dividers	3-10
3.5	Grounds & Voltage Labelling.....	3-15
3.6	Series Voltage Sources	3-17
3.7	Troubleshooting Series DC Circuits	3-21
3.8	A Glance Back.....	3-22

4. PARALLEL DC CIRCUITS

4.1	Parallel Resistors and Conductance	4-2
4.2	Parallel Circuits	4-6
4.3	Kirchhoff's Current Law (KCL).....	4-7
4.4	Changing Parallel Resistances	4-9
4.5	Current Dividers	4-10
4.6	Short Circuits.....	4-13
4.7	Troubleshooting Parallel DC Circuits.....	4-14
4.8	A Glance Back.....	4-16

5. SERIES-PARALLEL DC CIRCUITS

5.1	Determination of Series Components	5-2
5.2	Determination of Parallel Components.....	5-3
5.3	Circuit Reduction Techniques	5-5
5.4	Loaded Voltage Divider Circuits.....	5-13
5.5	Balanced Wheatstone Bridge Circuits	5-17
5.6	Troubleshooting Series-Parallel DC Circuits....	5-20
5.7	A Glance Back.....	5-22

6. ENERGY SOURCES

6.1	Available Energy Sources	6-2
6.2	Batteries.....	6-3
6.3	DC Voltage Source Representation	6-5
6.4	DC Current Source Representation.....	6-8
6.5	Connecting Multiple Sources	6-10
6.6	Transfer from Source to Load.....	6-12
6.7	Troubleshooting Circuits With Energy Sources	6-15
6.8	A Glance Back.....	6-16

7. SELECTED NETWORK ANALYSIS METHODS

7.1	Thévenin's Theorem.....	7-2
7.2	Norton's Theorem	7-7
7.3	Converting Sources	7-11
7.4	Superposition Analysis	7-12
7.5	Mesh Analysis	7-15
7.6	Nodal Analysis	7-20
7.7	A Glance Back.....	7-26

8. ELECTRIC FIELDS & CAPACITANCE

8.1	Electric Fields.....	8-2
8.2	Characteristics of Capacitance.....	8-3
8.3	Characteristics of Capacitors	8-7
8.4	Performance of Capacitors in Simple Circuits..	8-12
8.5	RC Charging Circuits	8-20
8.6	Troubleshooting Capacitive Circuits	8-28
8.7	A Glance Back.....	8-29

9. MAGNETIC FIELDS & INDUCTANCE

9.1	Magnetic Fields	9-2
9.2	Characteristics of Inductance.....	9-16
9.3	Characteristics of Inductors	9-18
9.4	Performance of Inductors in Simple Circuits....	9-21
9.5	RL Charging Circuits	9-25
9.6	Meter Movements.....	9-32
9.7	Ammeters, Voltmeters and Ohmmeters.....	9-33
9.8	Troubleshooting Inductive Circuits	9-37
9.9	A Glance Back.....	9-38